 


## Programmable Logic Devices – Laboratory

### 1. FPGA development board:

*Digilent Basys 3 (Xilinx Artix-7 FPGA)*



### 2. Install desgin software:

*Xilinx Vivado Design Suite WebPack (for 1a)*




<https://www.xilinx.com/products/design-tools/vivado/vivado-webpack.html>

### 3. Go through tutorial:

[https://www.xilinx.com/support/documentation/university/Vivado-Teaching/HDL-Design/2015x/VHDL/docs-pdf/Vivado\\_Tutorial.pdf](https://www.xilinx.com/support/documentation/university/Vivado-Teaching/HDL-Design/2015x/VHDL/docs-pdf/Vivado_Tutorial.pdf)

**Mini projects** (use buttons, switches and LEDs to test functionality):

1. Design **selected** circuit:

   

2. Design **selected** circuit:


- $T_4 = \{0, 1, 5, 7, 10, 12, 15\}$
- $Y = (AB + C)D$
- Truth table:

| X1 | X2 | X3 | X4 | Y |
|----|----|----|----|---|
| 0  | 0  | 0  | 0  | 0 |
| 0  | 0  | 0  | 1  | 0 |
| 0  | 0  | 1  | 0  | 0 |
| 0  | 0  | 1  | 1  | 1 |
| 0  | 1  | 0  | 0  | 1 |
| 0  | 1  | 0  | 1  | - |
| 0  | 1  | 1  | 0  | - |
| 0  | 1  | 1  | 1  | 1 |
| 1  | 0  | 0  | 0  | 0 |
| 1  | 0  | 0  | 1  | 1 |
| 1  | 0  | 1  | 0  | 0 |
| 1  | 0  | 1  | 1  | 0 |
| 1  | 1  | 0  | 0  | 0 |
| 1  | 1  | 0  | 1  | 1 |
| 1  | 1  | 1  | 0  | - |
| 1  | 1  | 1  | 1  | - |


3. Design **selected** code converter:

- NB to 1-hot converter
- NB to BCD converter
- NB 7-segment display converter (outputs connected to 7-segment display)


4. Design multiplexer 4x1.

 


5. Design demultiplexer 1x2.

 


6. Design 4-bit adder.

 

 7. Design combinational circuit, presented below, using previously designed circuit as components (VHDL port map instruction):



 8. Design **selected** flip-flop with asynchronous reset:



9. Design **selected** flip-flop with enable signal.



10. Design 8-bit shift register.  
 11. Design N-bit counter with synchronous reset (choose any N from 3 to 6).  
 12. Design modulo N counter (choose any N from 8 to 32).  
 13. Design frequency divider (divide input signal by 2/4/8 or 10).  
 14. Design selected state machine:  
 15. Write testbench for one previously designed circuit.

| Number of mini projects accepted | Grade |
|----------------------------------|-------|
| 8                                | 3     |
| 9-10                             | 3+    |
| 11-12                            | 4     |
| 13-14                            | 4+    |
| 15                               | 5     |